

Lecture 2: Bits and Switches

CS105: Great Insights in Computer Science
Michael L. Littman, Fall 2006

Clicker Registration

- Let's see if we can get it to work...

Grading

- In-class participation: 20%
- Biweekly HW: 25%
- Midterm: 25%
- Final (cumulative): 30%
 - Exam questions modeled on HW

Preface

- Hillis mentions “function abstraction”, which is close enough to what I called “reduction”.
- He also mentions “universality”, which is an application of this idea: Any model of computing can simulate any other. There is only one kind of computing.
- Computers empower our minds: *Imagination Machines*.
- Catchy, I think.

The Lowly Bit

- Chemistry has its molecules.
- Physics has its strings.
- Computer science has its bits.
- They are the smallest unit of information.
 - True (1, on)
 - False (0, off)



What's a "Bit"?


- Like "craptacular" (crap + spectacular) or "crumbelievable" (crumble + unbelievable); it is a *portmanteau*.
- It's a contraction of "binary digit", used by Claude Shannon, attributed to John Tukey.
- In our decimal (base ten) number system, a digit can be any of the ten values 0,...,9.
- In the binary (base 2) number system, a digit can be any of the two values 0 or 1.

Why a Bit?

- Bits have the property of being...
 - **simple:** There's no smaller discrete distinction to be made.
 - **powerful:** sequences of bits can represent seemingly anything!



0/1, Black/White

 - Escher created spectacular images with just a single distinction.
- "...God divided the light from the darkness." (Genesis Chapter 1, Line 4)



Bits Abound

  - Nearly everything has gone digital.
- Digital sound: groups of bits represent the acoustic intensity at discrete time points.
- Digital images: groups of bits represent the color at each particular discrete image location: pixel.



But There Are Lots of Them

- iPod: 60Gb. 1Gb = one billion bytes, each of which is 8 bits.
- Format uses 128 Kbps (kilobits or 1000 bits per second of sound).
- So, 62,500 minutes of sound or 15,000 songs at 4 minutes per song.
- Screen: 320x240 pixels, each of which stores 1 byte each of R,G,B intensity (24 bits). That's 76,800 pixels and 1.8M bits.
- At 30 frames per sec., that's 55.3 million bits per second or 144 min. of (quiet) video.



Logical Variable

- Bits are for more than just storage, they can store information in the form of logical or Boolean variables.
- A *logical variable* is something that we can imagine as being either True or False.
 - `todayIsWednesday = False`
 - `itIsDarkOut = False`
 - `IAmWearingSocks = True`

And, Or, Not

- The most important logical operations are **and**, **or**, and **not**.
 - `x and y` is True only if both `x` and `y` are True.
 - `x or y` is True only if either `x` or `y` are True.
 - `not x` is True only if `x` is False.
- A lot like their English meanings, but unambiguous.

Logical Expressions

- We can combine logical variables and operators into more complex expressions:
 - `todayIsWednesday and IAmWearingSocks = False`
 - `itIsDarkOut or IAmWearingSocks = True`
 - `not itIsDarkOut = True`



Quick Check

- `(not todayIsWednesday or itIsDarkOut) and (todayIsWednesday or not IAmWearingSocks) = ?`
 - A. False
 - B. True

Implementing Logic

- Clearly, our brains can handle these sorts of expressions.
- But, can we automate them?
- Yes, obviously, but let's start with a really simple way to do it before we move on to fancier stuff.

Simple Circuit

  


Switch A is either on or off making the light either on or off: $\text{lightOn} = A$.

Symbols:


battery 

switch 


bulb 

 ground (completes circuit) 

Multiple Switches

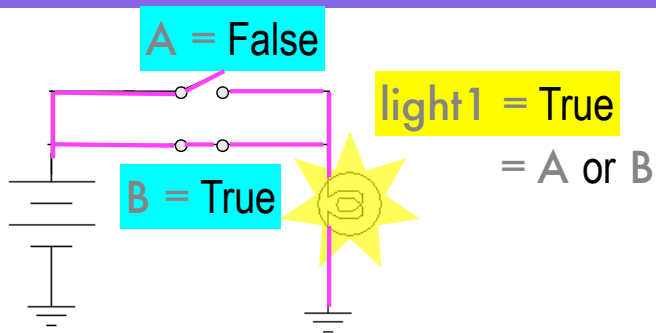


 Switches A and B are wired in *parallel*: either will light the bulb.



Switches C and D are wired in *series*: both are needed to light the bulb.

Multiple Circuits

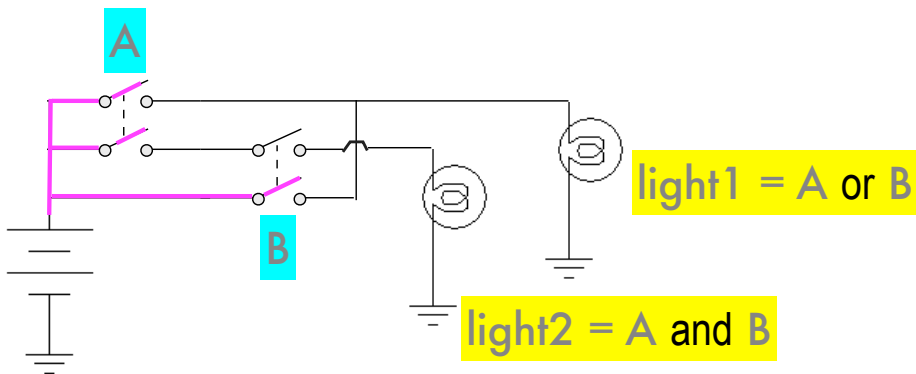

Special switches allow a single mechanical switch to control two circuits simultaneously.

miniNim


- There's a pile of objects, say 10.
- On her turn, a player can take away either one or two objects.
- Players alternate.
- The player to take the last object wins.



RRRRRRRRRRRR

Nim5Bot: Game Tree

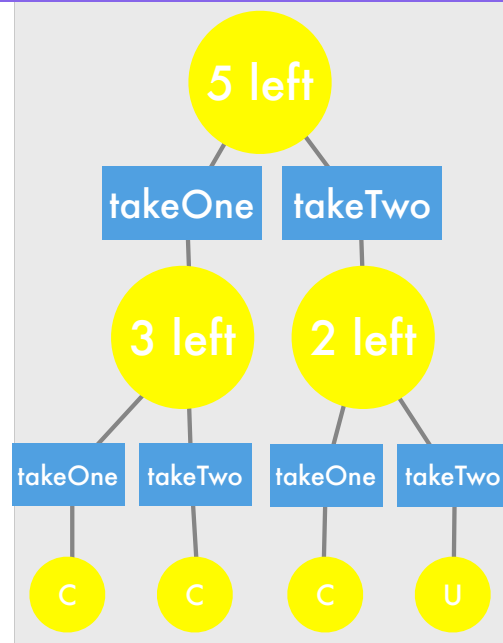- Let's start by considering the 5-object version.
- We'll design a strategy for the computer "C" to beat the user "U".



Backwards Induction

- There's a powerful idea here:
 - Many decision making problems can be solved optimally by reasoning backwards from the end of the game.
 - We know how to win from 1 or 2.
 - We use this to win from 4 or 5.
 - We use this to win from 7 or 8.
- Chess: removed pieces don't return.


Further Considerations

- To win miniNim: if possible, remove pieces to leave opponent with a multiple of 3.
 - Why does it work? We win if opponent has 3; if opponent has a multiple of 3, can leave her with next smaller multiple of 3.
- What if goal is to *not* take the last object?
- What if we can take 1, 2, or 3 objects per round? 2 or 3? 1 or 3? Is there a general rule?

Complete Nim5 Logic

- $\text{fiveLeft} = \text{True}$
- $\text{threeLeft} = \text{takeOne}_1$
- $\text{twoLeft} = \text{takeTwo}_1$
- $\text{C-Win} = (\text{threeLeft} \text{ and } (\text{takeOne}_2 \text{ or } \text{takeTwo}_2))$
or $(\text{twoLeft} \text{ and } \text{takeOne}_2)$
- $\text{U-Win} = \text{twoLeft} \text{ and } \text{takeTwo}_2$

Nim5 Circuit

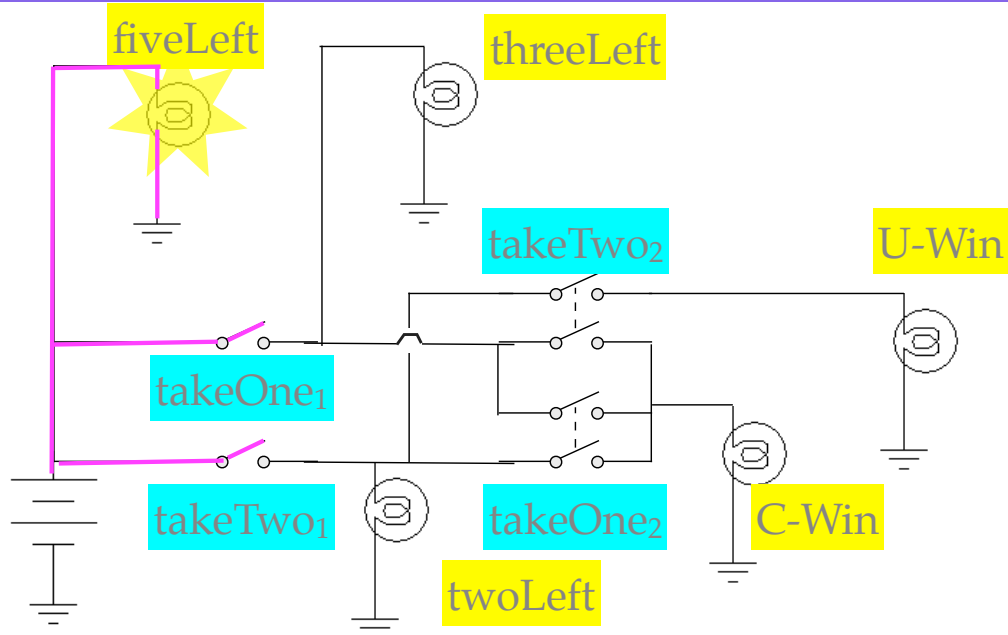

Let's Play!

- <http://www.cs.rutgers.edu/~mlittman/courses/cs105-06b/python/>
- nim5.py
- nim10.py

Complete Nim 10 Logic

```
tenLeft[1] = True
eightLeft[2] = takeOneSwitch[1]
sixLeft[2] = takeTwoSwitch[1]
sixLeft[3] = eightLeft[2] and takeOneSwitch[2]
fourLeft[3] = eightLeft[2] and takeTwoSwitch[2]
moveTwo = takeOneSwitch[2] or takeTwoSwitch[2]
threeLeft[3] = sixLeft[2] and moveTwo
moveThree = takeOneSwitch[3] or takeTwoSwitch[3]
threeLeft[4] = sixLeft[3] and moveThree
twoLeft[4] = fourLeft[3] and takeOneSwitch[3]
winFourA = threeLeft[3] and moveThree
winFourB = fourLeft[3] and takeTwoSwitch[3]
IWin[4] = winFourA or winFourB
moveFour = takeOneSwitch[4] or takeTwoSwitch[4]
winFiveA = twoLeft[4] and takeOneSwitch[4]
winFiveB = threeLeft[4] and moveFour
IWin[5] = winFiveA or winFiveB
youWin[5] = twoLeft[4] and takeTwoSwitch[4]
```


What a Headache!

- I tried to create the circuit diagram for Nim10 and couldn't do it. Why?
 - Since some switches are used in multiple places, needs more than a double-throw switch.
 - Since values are reused, hard to keep track of different circuits.
 - Appears to need a separate circuit for each output: Gets too complex too fast.

Need a New Approach


- Let's consider an alternate way of defining "and" and "or".
 - Makes simple things more complex.
 - Makes complex things *much* simpler!
- That's a tradeoff we can deal with.

Switch Switcher

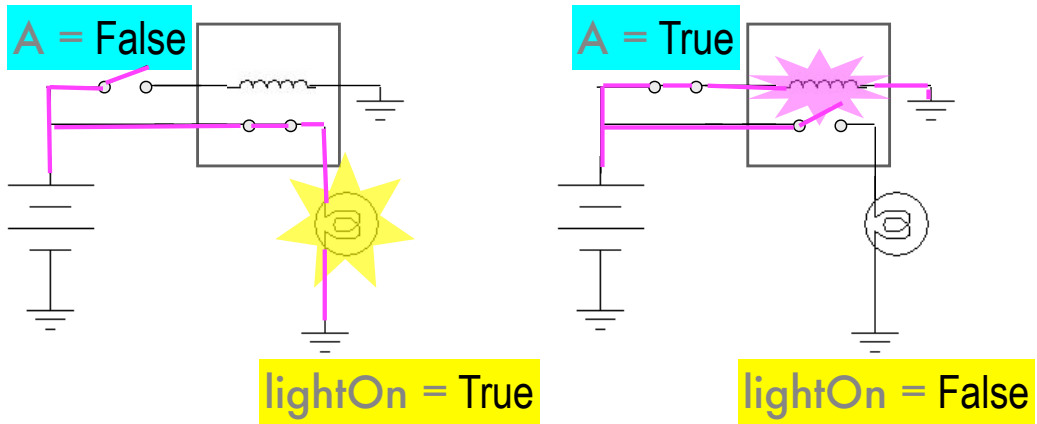


Before, we used switches to control the flow of current; now, we will use current (via electromagnetism) to control switches (which control the flow of current)!


Relay Circuit: A=F, B=F

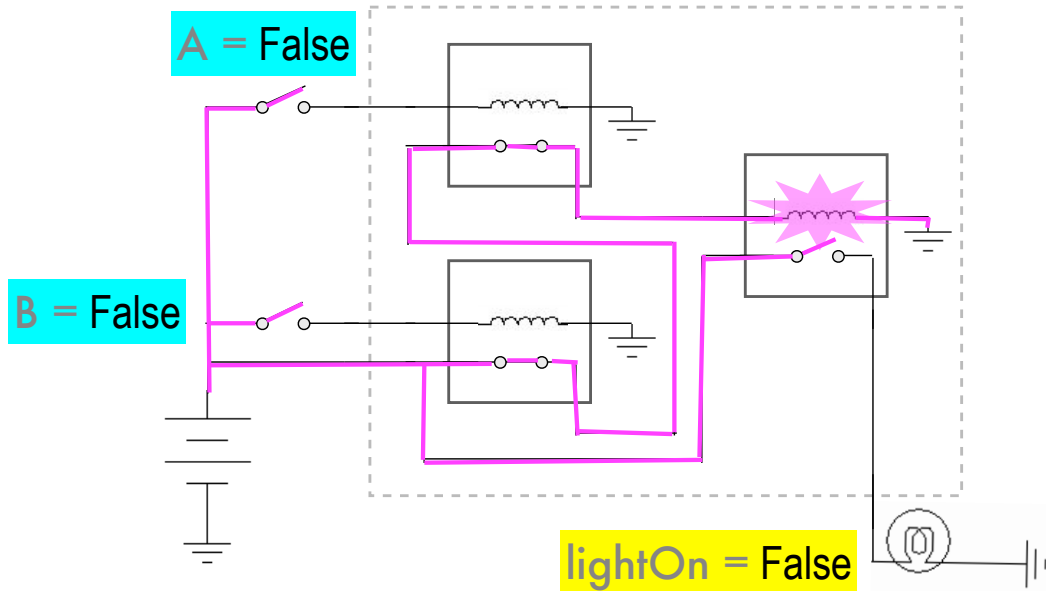


Relay Circuit: A=F, B=T

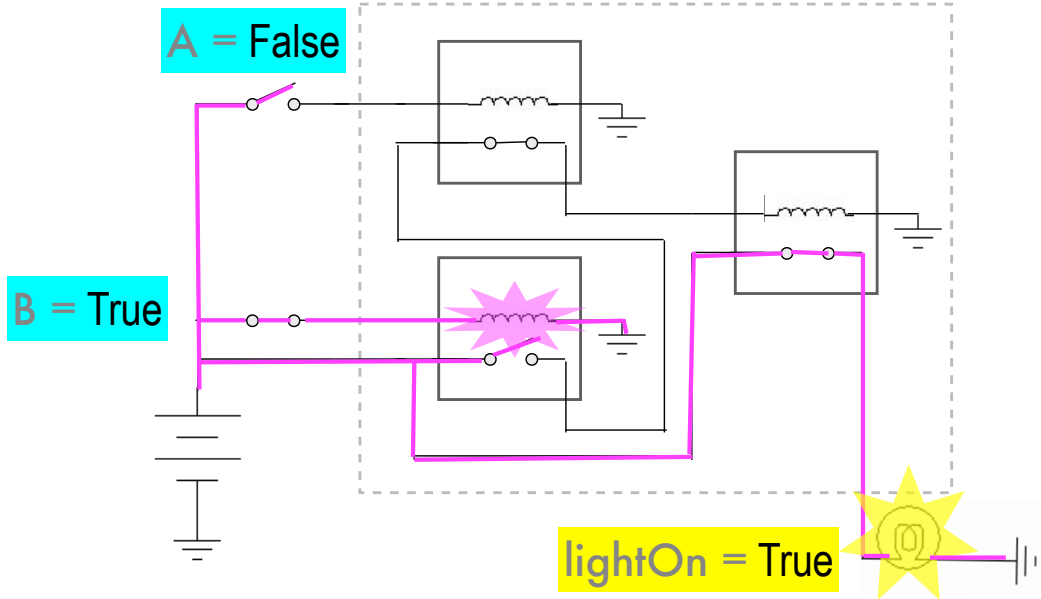

Relay Circuit: A=T, B=F

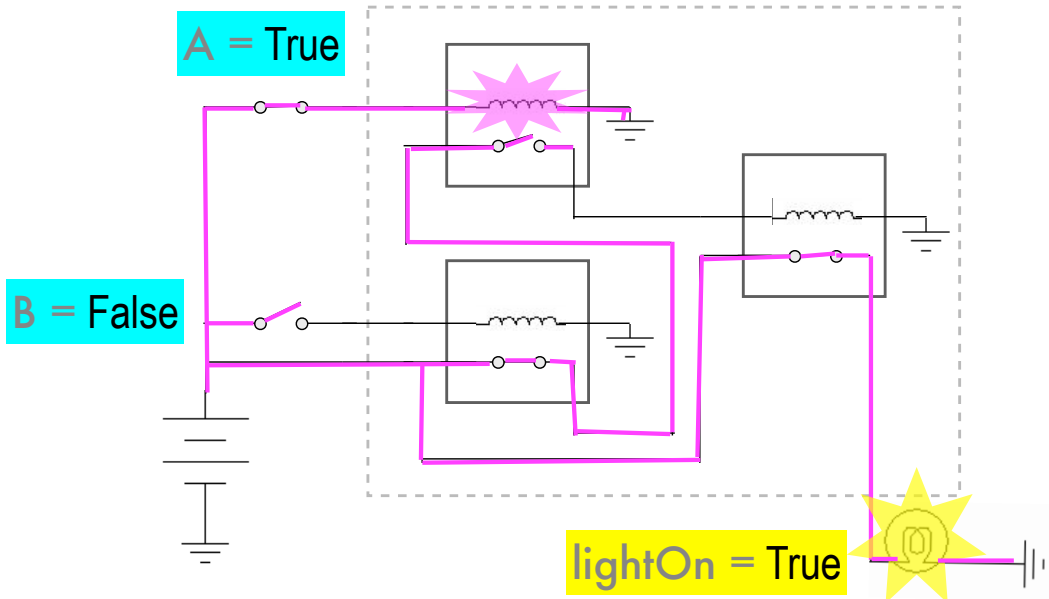


Relay Circuit: A=T, B=T

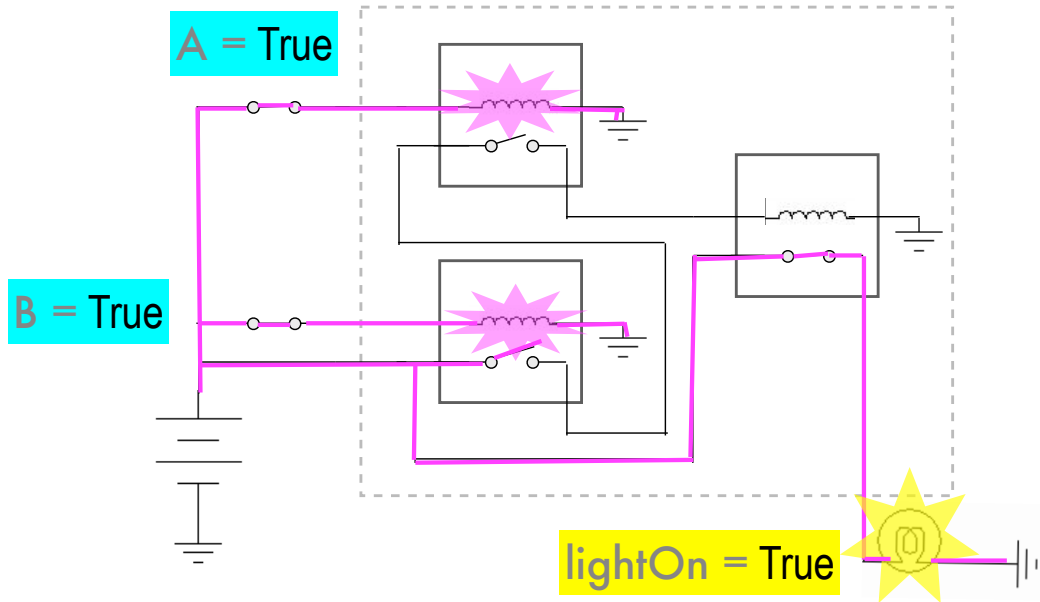

What Is This Thing?

A	B	C
False	False	False
False	True	True
True	False	True
True	True	True

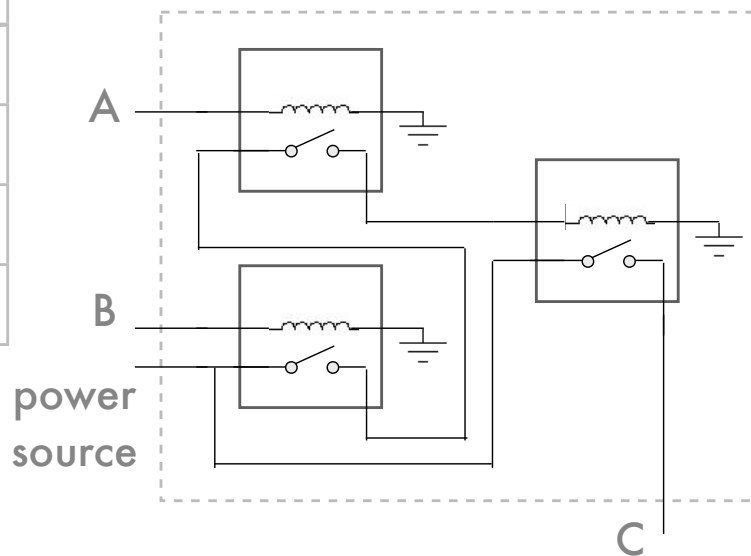
- A. "or" gate
- B. "and" gate
- C. "not" gate
- D. none of these



What Is This Thing?

A	B	C
False	False	False
False	True	True
True	False	True
True	True	True

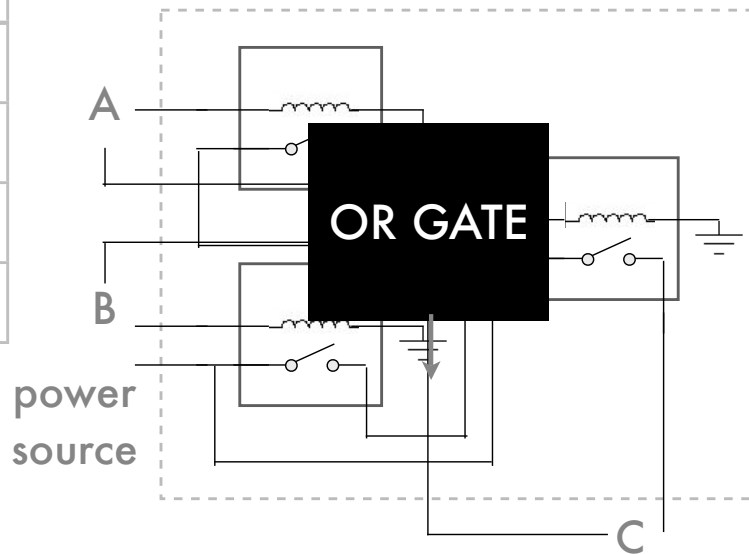It's an "or gate":
used to compute
the "or" of two
inputs.



And One For "Not"


- We saw several slides ago that a single relay "inverts" its input signal, turning a True to a False and vice versa.
- These output summaries are known as "truth tables".

A	B
False	True
True	False



Abstraction: The Black Box

 
- Our new relayed-based “or” and “not” gates take current, not switches, as input.
- As a result, they are easier to chain together.
- The original switch-based scheme did not support this kind of modularity.




A Third Black Box

A	B	C
False	False	False
False	True	False
True	False	False
True	True	True

 It's an “and gate”:
a black box built
out of other black
boxes!



Simplified Nim5 Circuit

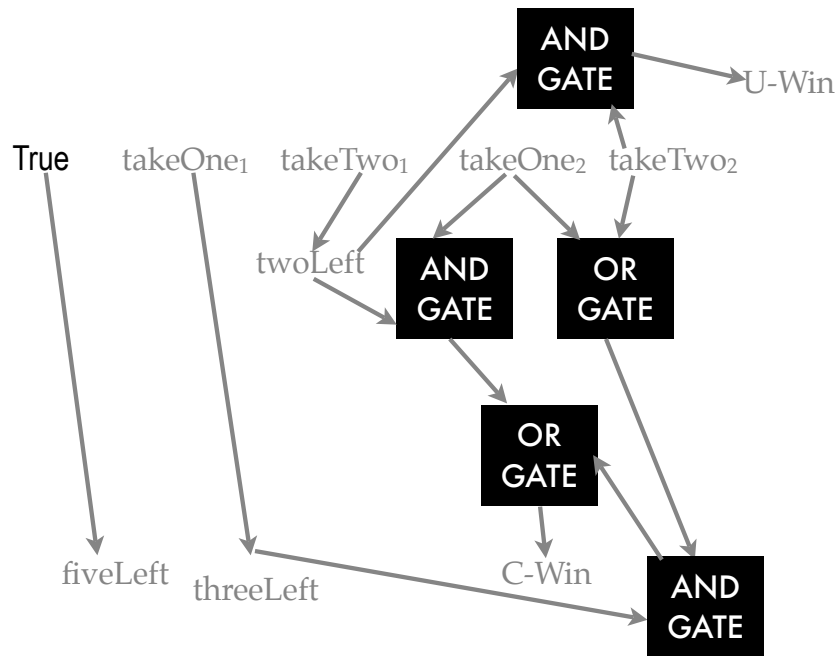

Next Time

- We'll talk about some other ways to make "or" and "not" gates.
- We'll use gates to create a bunch of other black boxes, building complexity as we go.
- Read Hillis, remaining Sections of Chapter 1.
- Chapter 2 up to and including "Logical Functions".